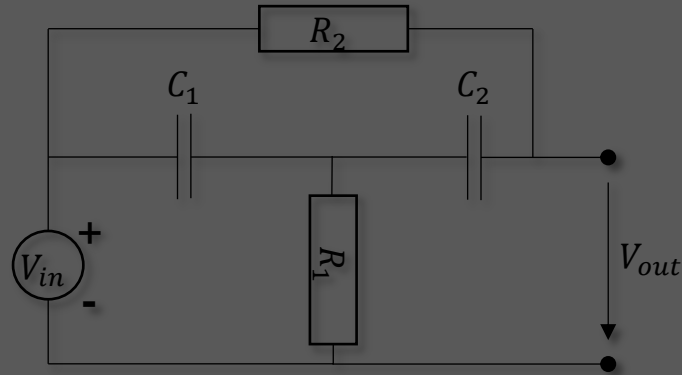


Modeling & Simulation of a Notch Filter using solidThinking *Activate*




Notch Filter

A notch filter circuit is used to remove an unwanted frequency or range of frequencies from a signal.

Our notch frequency is designed at $\approx 100 \frac{rad}{s}$.

Targets

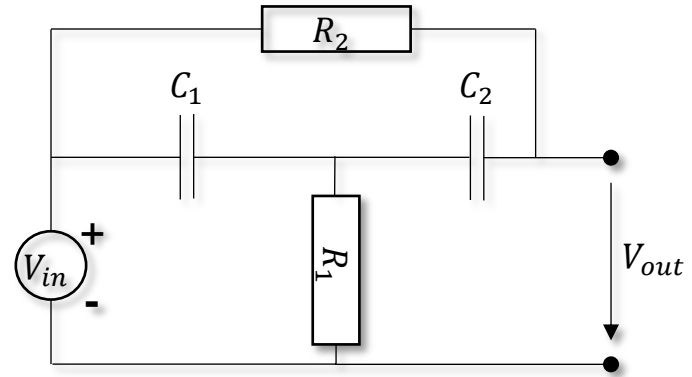- Learn how to...
 - ... build a block diagram model a second order circuit
 - ... plot a frequency sweep response of the circuit



Creation and Simulation of a Notch Filter

Theoretical background and how to implement it using *Activate*

Step 1: Construction of equations

Step 2: Implementation using *Activate*

Step 3: Validation of the results

Step 1: Construction of equations


- *Kirchhoff's nodal rule:*

- At any node: $\sum_{s=1}^m i_s = 0$

- *Integral Causality Equations:*


- *Objective: Avoid differentiating to improve numerical stability*

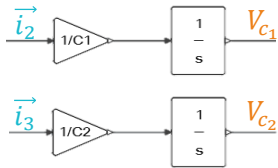- $V_{C_j} = \frac{1}{C_j} \int_0^t i_j dt$





- *Kirchhoff's mesh rule:*

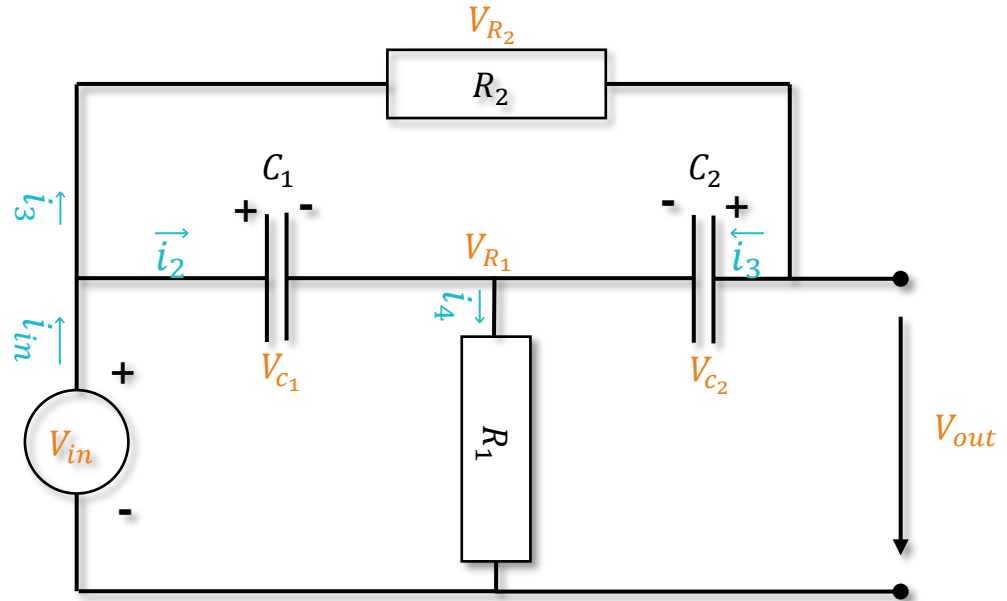- In a closed loop: $\sum_{k=1}^n V_k = 0$







Step 2: Implementation using Activate

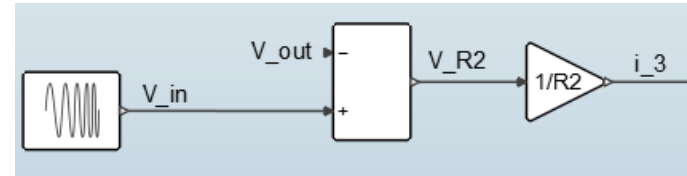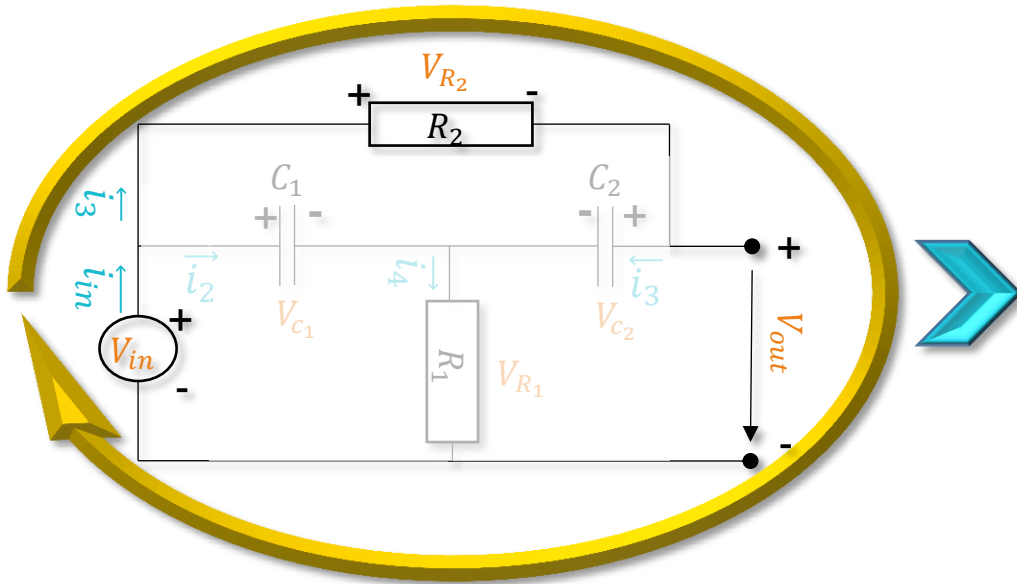- Kirchhoff's mesh rule: $-V_{in} + V_{R_2} + V_{out} = 0$





Step 2: Implementation using Activate

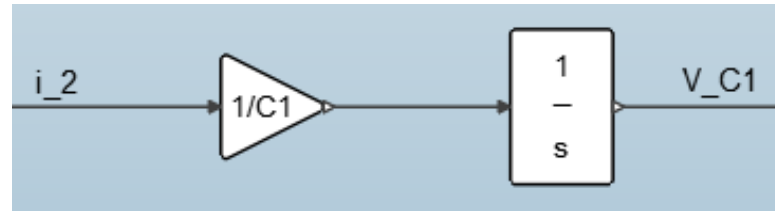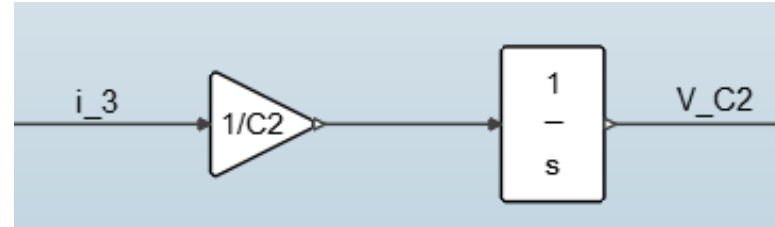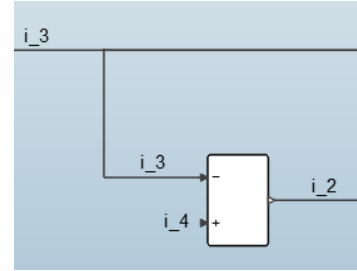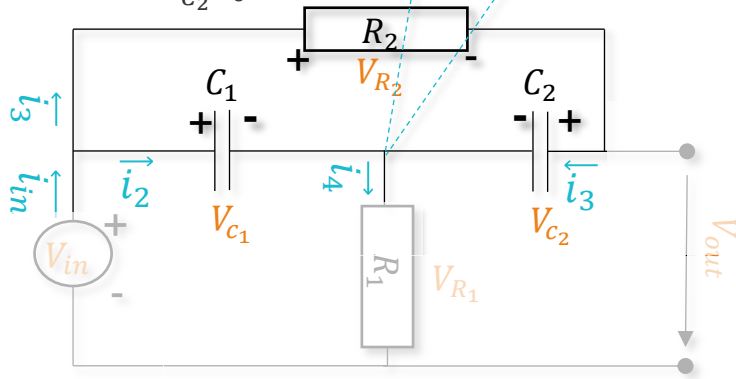- Kirchhoffs nodal rule: $i_2 + i_3 = i_4$
- Integral Causality Equations:
 - $V_{C_1} = \frac{1}{C_1} \int_0^t i_2 dt$
 - $V_{C_2} = \frac{1}{C_2} \int_0^t i_3 dt$



Step 2: Implementation using Activate

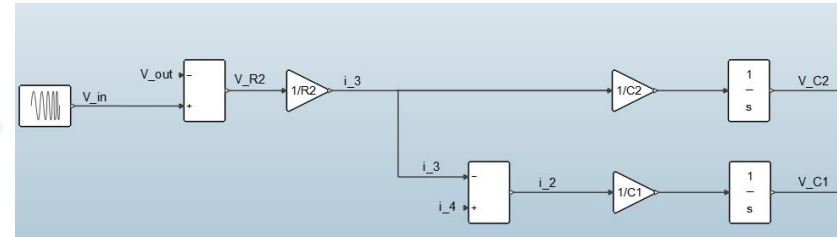
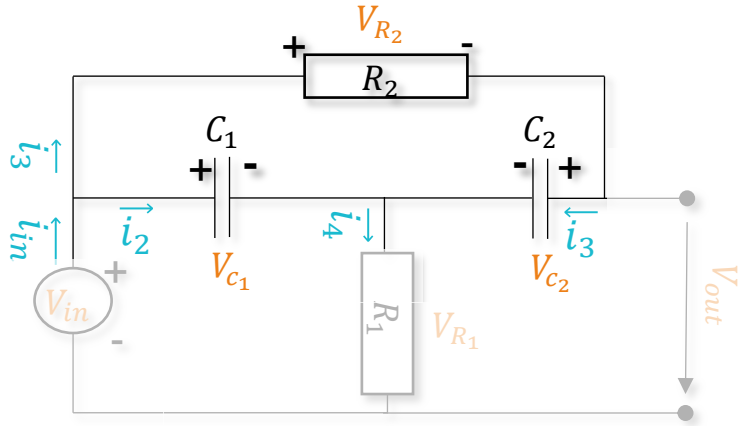
- Model so far:
 - The current i_4 and voltage V_{out} are still unknown.



Step 2: Implementation using Activate



- *Kirchhoff's* mesh rule:

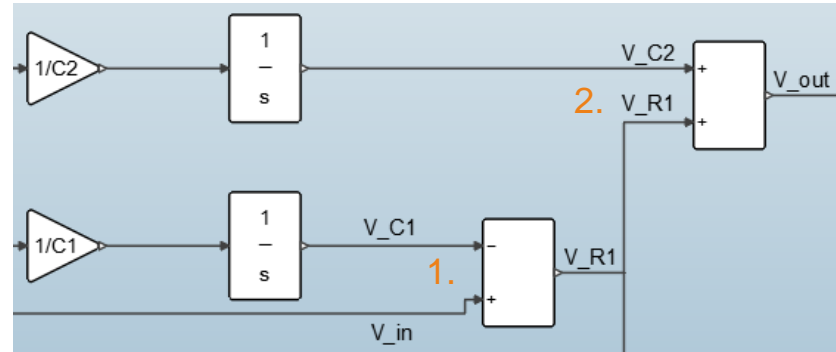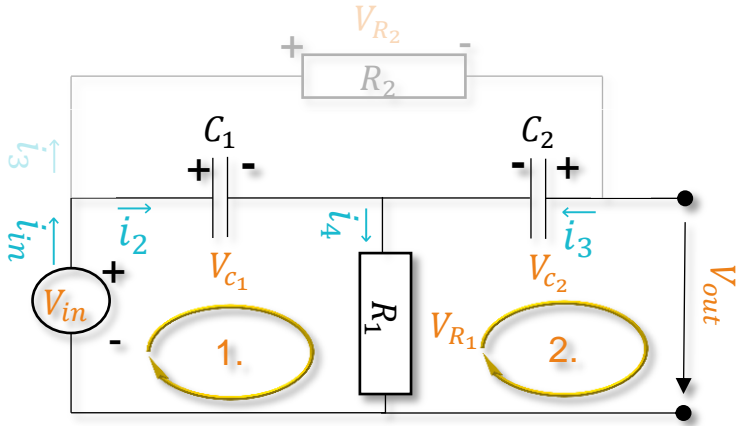- 1. $-V_{in} + V_{C_1} + V_{R_1} = 0 \Leftrightarrow V_{R_1} = V_{in} - V_{C_1}$
- 2. $V_{R_1} + V_{C_2} - V_{out} = 0 \Leftrightarrow V_{out} = V_{C_2} + V_{R_1}$




Step 2: Implementation using Activate

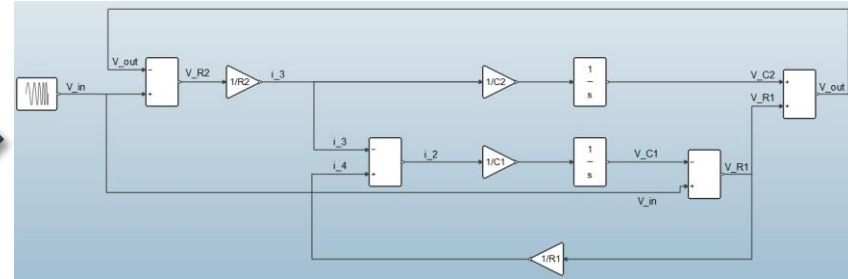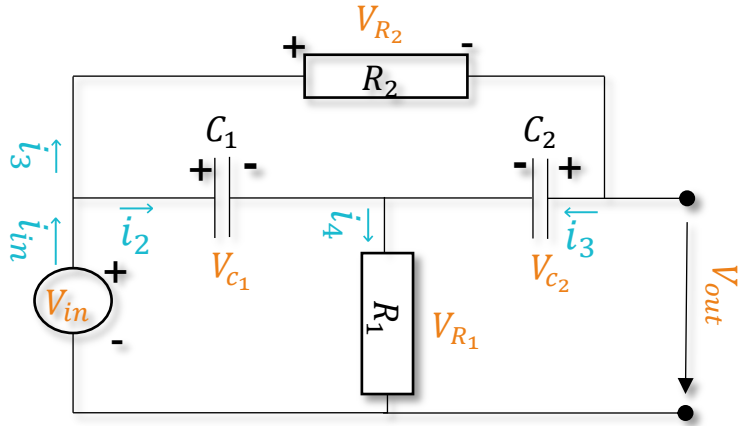- Complete model:
- Feed back V_{out} and i_4 .
 - $i_4 = \frac{1}{R_1} V_{R1}$



Step 2: Implementation using Activate

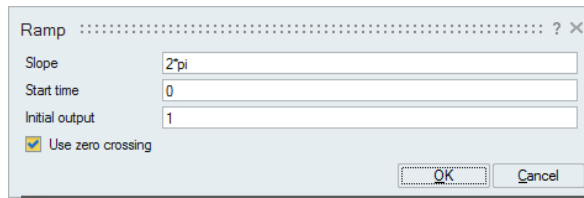- Plotting the frequency vs. the output voltage V_{out} as a sweep frequency response.



Frequency [Hertz]


V_{out}




- Parameters to notch out a frequency of $\approx 100\text{Hz}$:
 - $R_1 = 1$
 - $R_2 = 100$
 - $C_1 = 0.001$
 - $C_2 = 0.001$
 - $V_{in} = 1$

Step 2: Implementation using *Activate*

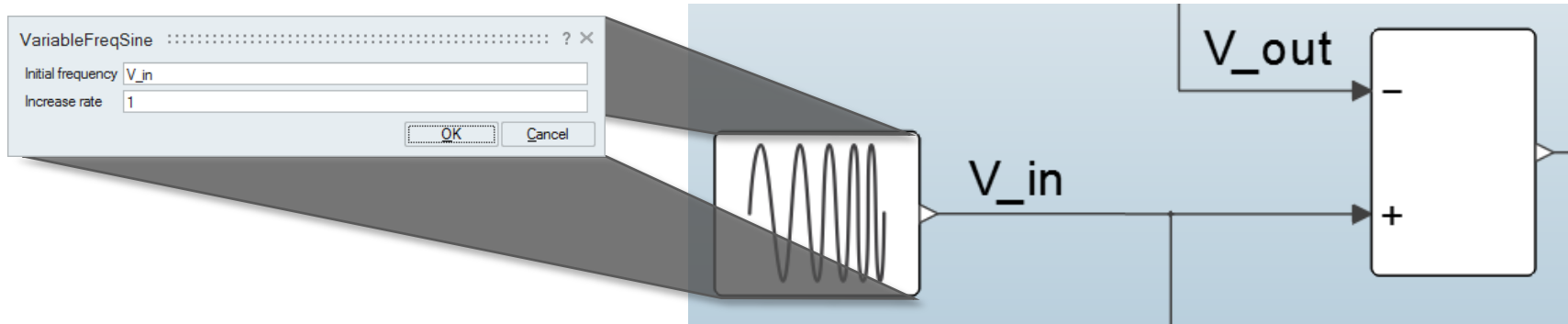- Plotting the frequency vs. the output voltage V_{out} as a sweep frequency response.




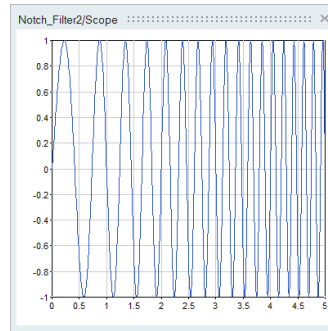- This “*VariableFreqSine*” block plots a Sinewave starting with a frequency of 1 Hz and increases itself with $1\frac{\text{rad}}{\text{s}}$. →



Step 3: Validation of the results

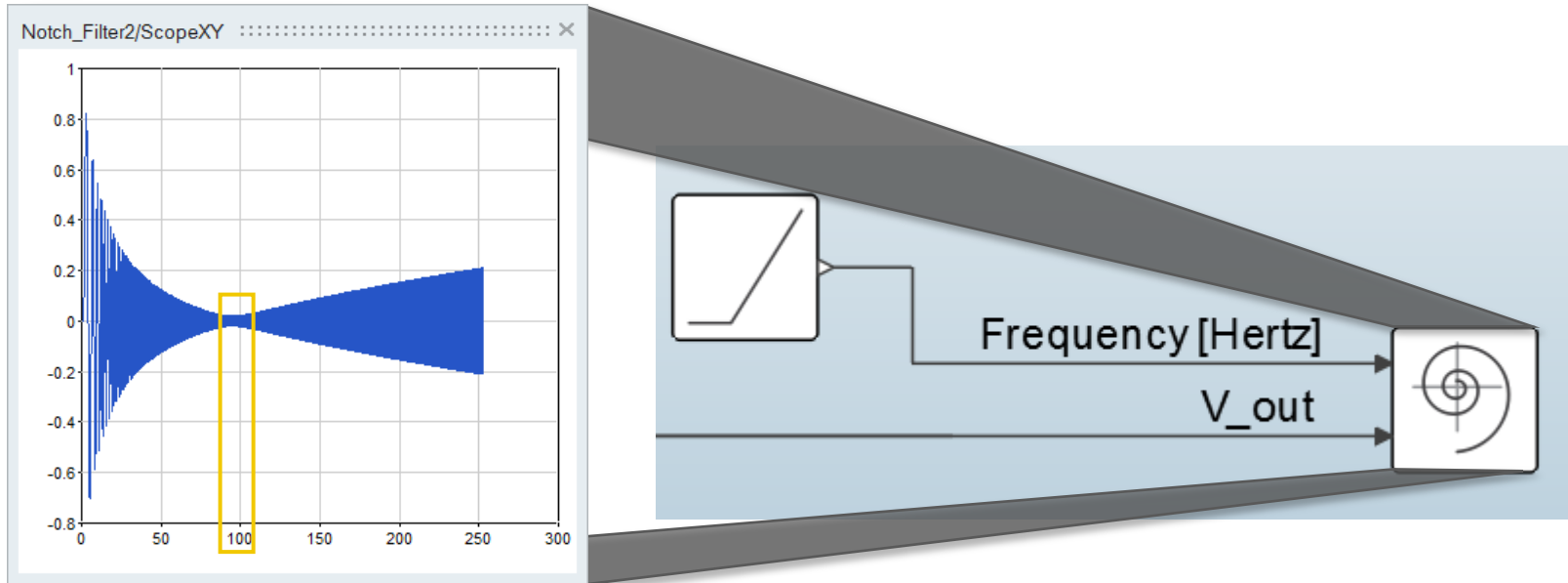- Plotting the frequency vs. the output voltage V_{out} as a sweep frequency response.



- The frequency near to 100 Hz is notched out by this electrical circuit.